

Verilog for Sequential Circuits

What will we learn?


- **Short summary of Verilog Basics**
- **Sequential Logic in Verilog**
- **Using Sequential Constructs for Combinational Design**
- **Finite State Machines**

Summary: Defining a module

- A module is the main building block in Verilog
- We first need to declare:
 - Name of the module
 - Types of its connections (input, output)
 - Names of its connections



Summary: Defining a module

 

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
  
endmodule
```

Summary: What if we have busses ?

- You can also define multi-bit busses.


- [range_start : range_end]

```
input  [31:0] a; // a[31], a[30] .. a[0]
output [15:8] b1; // b1[15], b1[14] .. b1[8]
output [7:0]  b2; // b2[7], b2[6] .. b1[0]
input          clk;
```

Structural HDL Example

Short Instantiation
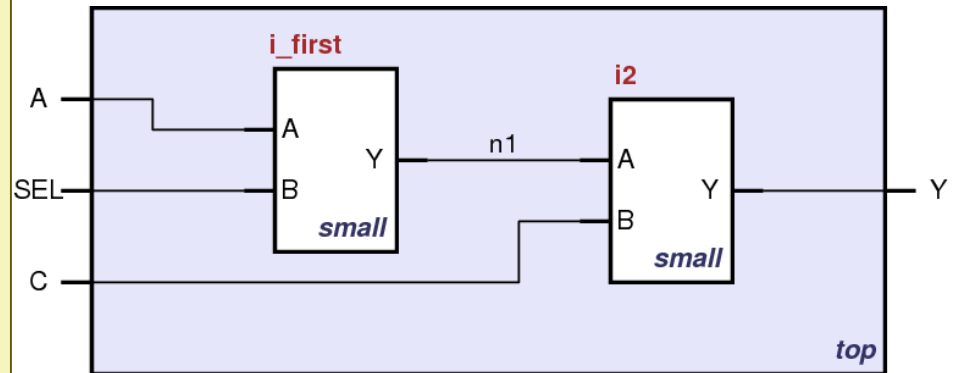
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // alternative  
  small i_first ( A, SEL, n1 );  
  
  /* Shorter instantiation,  
     pin order very important */  
  
  // any pin order, safer choice  
  small i2 ( .B(C),  
             .Y(Y),  
             .A(n1) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Summary: Bitwise Operators

```
module gates(input  [3:0]  a, b,  
              output [3:0] y1, y2, y3, y4, y5);  
  
    /* Five different two-input logic  
       gates acting on 4 bit busses */  
  
    assign y1 = a & b;      // AND  
    assign y2 = a | b;      // OR  
    assign y3 = a ^ b;      // XOR  
    assign y4 = ~(a & b);   // NAND  
    assign y5 = ~(a | b);   // NOR  
  
endmodule
```

Summary: Conditional Assignment

- **? :** is also called a **ternary operator** because it operates on 3 inputs:

- s
- d1
- d0.

```
module mux2(input  [3:0] d0, d1,  
            input          s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```


Summary: How to Express numbers ?

N' Bxx

8' b0000_0001

- **(N) Number of bits**

- Expresses how many bits will be used to store the value

- **(B) Base**

- Can be b (binary), h (hexadecimal), d (decimal), o (octal)

- **(xx) Number**

- The value expressed in base, apart from numbers it can also have X and Z as values.
- Underscore _ can be used to improve readability

Summary: Verilog Number Representation

Verilog	Stored Number	Verilog	Stored Number
4'b1001	1001	4'd5	0101
8'b1001	0000 1001	12'hFA3	1111 1001 0011
8'b0000_1001	0000 1001	8'o12	00 001 010
8'bxX0X1zZ1	XX0X 1ZZ1	4'h7	0111
'b01	0000 .. 0001	12'h0	0000 0000 0000

Precedence of Operations in Verilog

Highest	~	NOT
	*, /, %	mult, div, mod
	+, -	add,sub
	<<, >>	shift
	<<<, >>>	arithmetic shift
	<, <=, >, >=	comparison
	==, !=	equal, not equal
	&, ~&	AND, NAND
	^, ~^	XOR, XNOR
	, ~	OR, NOR
Lowest	?:	ternary operator

Sequential Logic in Verilog

- **Define blocks that have memory**
 - Flip-Flops, Latches, Finite State Machines
- **Sequential Logic is triggered by a 'CLOCK' event**
 - Latches are sensitive to level of the signal
 - Flip-flops are sensitive to the transitioning of clock
- **Combinational constructs are not sufficient**
 - We need new constructs:
 - `always`
 - `initial`


always Statement, Defining Processes

```
always @ (sensitivity list)  
    statement;
```

- Whenever the event in the sensitivity list occurs, the statement is executed

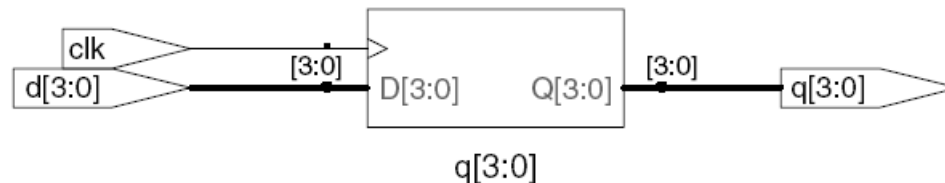Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```



Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- The posedge defines a rising edge (transition from 0 to 1).
- This process will trigger only if the **clk signal rises**.
- Once the clk signal rises: the value of **d** will be copied to **q**

Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;           // pronounced “q gets d”  
  
endmodule
```

- **‘assign’ statement is not used within always block**
- **The <= describes a ‘non-blocking’ assignment**
 - We will see the difference between ‘blocking assignment’ and ‘non-blocking’ assignment in a while

Example: D Flip-Flop

```
module flop(input          clk,  
            input [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <= d;                // pronounced “q gets d”  
  
endmodule
```

- Assigned variables need to be declared as **reg**
- The name reg does not necessarily mean that the value is a register. (It could be, it does not have to be).
- We will see examples later

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0;    // when reset
    else               q <= d;    // when clk
  end
endmodule
```

■ In this example: two events can trigger the process:

- A *rising edge* on clk
- A *falling edge* on reset

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,  
                input          reset,  
                input  [3:0] d,  
                output reg [3:0] q);  
  
  always @ (posedge clk, negedge reset)  
  begin  
    if (reset == '0') q <= 0;    // when reset  
    else               q <= d;    // when clk  
  end  
endmodule
```

- For longer statements a begin end pair can be used
 - In this example it was not necessary
- The always block is *highlighted*

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input [3:0] d,
                output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0; // when reset
    else               q <= d; // when clk
  end
endmodule
```

- **First reset is checked, if reset is 0, q is set to 0.**
 - This is an 'asynchronous' reset as the reset does not care what happens with the clock
- **If there is no reset then normal assignment is made**

D Flip-Flop with Synchronous Reset

```
module flop_sr (input          clk,
                input          reset,
                input [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk)
    begin
        if (reset == '0') q <= 0;    // when reset
        else               q <= d;    // when clk
    end
endmodule
```

- The process is only sensitive to clock
 - Reset *only happens* when the *clock rises*. This is a 'synchronous' reset
- A small change, has a large impact on the outcome

D Flip-Flop with Enable and Reset

```
module flop_ar (input          clk,
                input          reset,
                input          en,
                input [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk. negedge reset)
    begin
        if (reset == '0') q <= 0;    // when reset
        else if (en)      q <= d;    // when en AND clk
    end
endmodule
```


- A flip-flop with enable and reset

- Note that the en signal is *not* in the sensitivity list

- Only when “clk is rising” *AND* “en is 1” data is stored

 Example: D Latch

```
module latch (input          clk,  
              input    [3:0] d,  
              output reg [3:0] q);  
  
  always @ (clk, d)  
    if (clk) q <= d;      // latch is transparent when  
                          // clock is 1  
  
endmodule
```



Summary: Sequential Statements so far

- Sequential statements are within an **'always'** block
- The sequential block is triggered with a change in the sensitivity list
- Signals assigned within an always must be declared as **reg**
- We use **<=** for (non-blocking) assignments and do not use **'assign'** within the always block.

Summary: Basics of always Statements

```
module example (input          clk,
                 input    [3:0] d,
                 output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;            // first FF array

    assign normal = ~ special;    // simple assignment

    always @ (posedge clk)
        q <= normal;             // second FF array
endmodule
```

- You can have many always blocks

Why does an always Statement Memorize?

```
module flop (input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (posedge clk)  
    begin  
        q <= d;    // when clk rises copy d to q  
    end  
endmodule
```

- This statement describes what happens to signal q
- ... but what happens when clock is not rising?

Why does an always Statement Memorize?


```
module flop (input          clk,  
             input    [3:0] d,  
             output reg [3:0] q);  
  
    always @ (posedge clk)  
    begin  
        q <= d;    // when clk rises copy d to q  
    end  
endmodule
```

- This statement describes what happens to signal q
- ... but what happens when clock is not rising?
- The value of q is preserved (memorized)


Finite State Machines (FSMs)

- Each FSM consists of three separate parts:

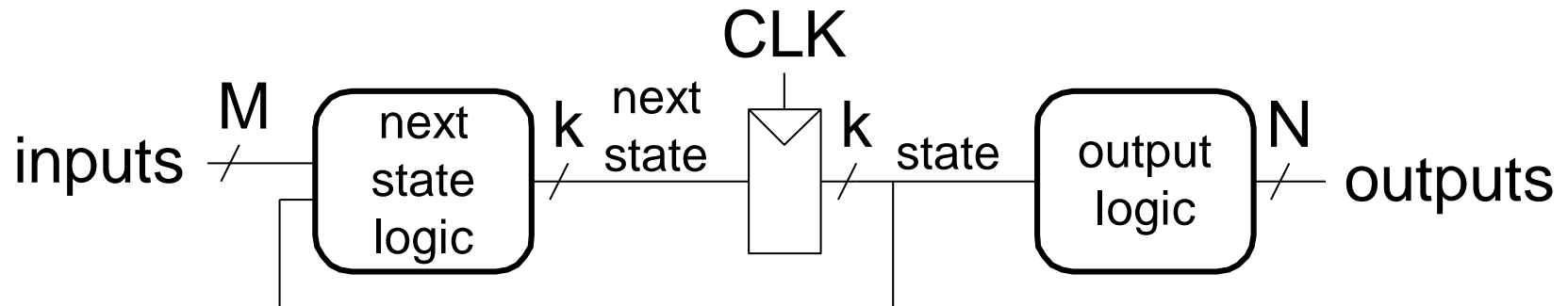- next state logic
- state register
- output logic



FSM Example: Divide by 3

 

FSM in Verilog, Definitions

```
module divideby3FSM (input clk,  
                    input reset,  
                    output q);  
  
    reg [1:0] state, nextstate;  
  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;
```

- We define state and nextstate as 2-bit reg
- The parameter descriptions are optional, it makes reading easier

FSM in Verilog, State Register

```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the state register (memorizing process)
- Sensitive to only clk, reset
- In this example reset is active when '1'

FSM in Verilog, Next State Calculation

```
// next state logic
always @ (*)
  case (state)
    S0:      nextstate = S1;
    S1:      nextstate = S2;
    S2:      nextstate = S0;
    default: nextstate = S0;
  endcase
```

- Based on the value of state we determine the value of nextstate
- An `always .. case` statement is used for simplicity.

FSM in Verilog, Output Assignments

```
// output logic  
assign q = (state == S0);
```

- In this example, output depends only on state
 - Moore type FSM
- We used a simple combinational assign

FSM in Verilog, Whole Code

```
module divideby3FSM (input clk, input reset, output q);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;

    always @ (posedge clk, posedge reset) // state register
        if (reset) state <= S0;
        else state <= nextstate;
    always @ (*) // next state logic
        case (state)
            S0: nextstate = S1;
            S1: nextstate = S2;
            S2: nextstate = S0;
            default: nextstate = S0;
        endcase
    assign q = (state == S0); // output logic
endmodule
```