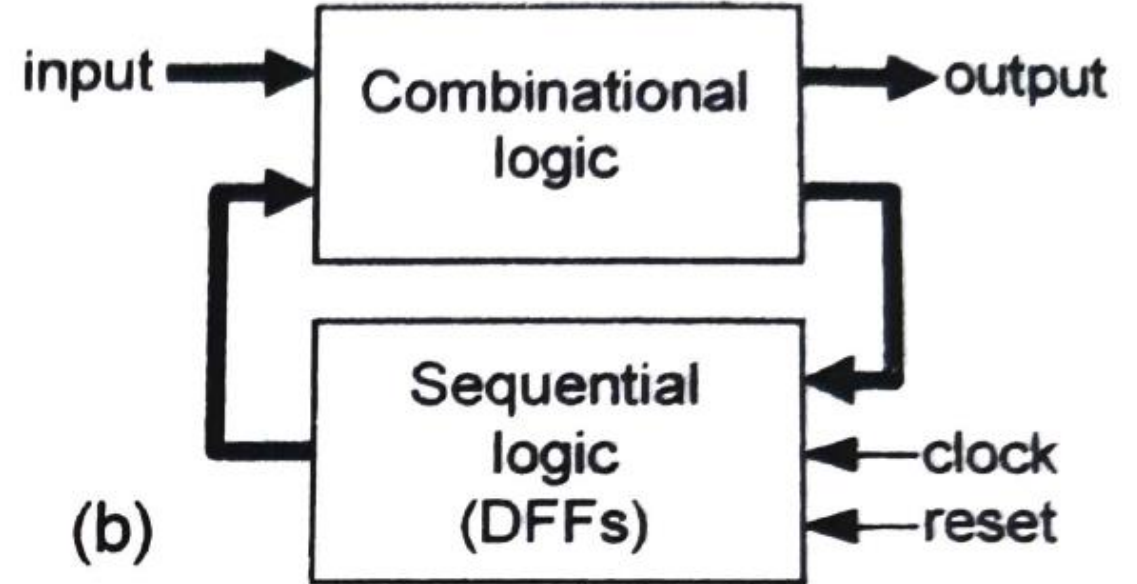
 


Concurrent and sequential statements (designing combinational circuits)



While concurrent code is intended only for the design of combinational circuits, sequential code can be used indistinctly to design both sequential and combinational circuits.

~~Concurrent~~

Today's agenda.

→ Statements for concurrent
Code

~~When select statement~~

— When-else Statement

— With-Select-When Statement

→ Statements for
Sequential Code

— If-else Statement

— Case Statement

When-else statement

```
assignment_expression WHEN conditions ELSE  
    assignment_value WHEN conditions ELSE  
    ...;
```

When-else statement

- Syntax

```
output_signal <= expa when cond1 else  
                    expb when cond2 else  
                    .....  
                    expx when condx else  
                    expy;
```

output_signal: output(s),
condi: condition in terms of inputs
expi: expression in terms of inputs

With-select-when statement

```
WITH identifier SELECT  
    assignment_expression WHEN values,  
    assignment_value WHEN values,  
    ...;
```

Syntax → With-select-when statement

```
with sel select  
output_signal <= expra when choices,  
               exprb when choices,  
               .....  
               exprx when others;
```

 

Sequential statement: If-elsif-else

```
[label:] IF conditions THEN  
    assignments;  
ELSIF conditions THEN  
    assignments;  
...  
ELSE  
    assignments;  
END IF [label];
```


Sequential : Case statements

```
[label:] CASE expression IS  
    WHEN value => assignments;  
    WHEN value => assignments;  
    ...  
END CASE;
```

Case study: 4:1 MUX



Code examples

Concurrent code → when-else

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 entity mux1 is
24     Port ( x1 : in  STD_LOGIC_VECTOR (3 downto 0);
25           x2 : in  STD_LOGIC_VECTOR (3 downto 0);
26           x3 : in  STD_LOGIC_VECTOR (3 downto 0);
27           x4 : in  STD_LOGIC_VECTOR (3 downto 0);
28           sel : in  STD_LOGIC_VECTOR (1 downto 0);
29           y : out  STD_LOGIC_VECTOR (3 downto 0));
30 end mux1;
31
32
33 architecture concurrent1 of mux1 is
34
35 begin
36 y <= x1 when sel="00" else
37     x2 when sel="01" else
38     x3 when sel="10" else
39     x4 when sel="11" else "XXXXX";
40 end concurrent1;
```

Concurrent code → with-select-when

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22
23 entity mux2 is
24     Port ( x1 : in  STD_LOGIC_VECTOR (3 downto 0);
25           x2 : in  STD_LOGIC_VECTOR (3 downto 0);
26           x3 : in  STD_LOGIC_VECTOR (3 downto 0);
27           x4 : in  STD_LOGIC_VECTOR (3 downto 0);
28           sel : in  STD_LOGIC_VECTOR (1 downto 0);
29           y : out  STD_LOGIC_VECTOR (3 downto 0));
30 end mux2;
31
32 architecture concurrent2 of mux2 is
33 begin
34     with sel select
35     y <= x1 when "00",
36         x2 when "01",
37         x3 when "10",
38         x4 when "11",
39         "XXXX" when others;
40 end concurrent2;
```

Sequential
code →
if-else
statements

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 entity mux3 is
23     Port ( x1 : in  STD_LOGIC_VECTOR (3 downto 0);
24           x2 : in  STD_LOGIC_VECTOR (3 downto 0);
25           x3 : in  STD_LOGIC_VECTOR (3 downto 0);
26           x4 : in  STD_LOGIC_VECTOR (3 downto 0);
27           sel : in  STD_LOGIC_VECTOR (1 downto 0);
28           y : out  STD_LOGIC_VECTOR (3 downto 0));
29 end mux3;
30
31 architecture sequential1 of mux3 is
32 begin
33 process (x1,x2,x3,x4,sel)
34 begin
35 if sel="00" then
36     y<=x1;
37 elsif sel="01" then
38     y<=x2;
39 elsif sel="10" then
40     y<=x3;
41 elsif sel="11" then
42     y<=x4;
43 else
44     y<="XXXXX";
45 end if;
46 end process;
47 end sequential1;
```

Sequential
code →
Case
statement

```
20 library IEEE;
21 use IEEE.STD_LOGIC_1164.ALL;
22 entity mux4 is
23     Port ( x1 : in  STD_LOGIC_VECTOR (3 downto 0);
24           x2 : in  STD_LOGIC_VECTOR (3 downto 0);
25           x3 : in  STD_LOGIC_VECTOR (3 downto 0);
26           x4 : in  STD_LOGIC_VECTOR (3 downto 0);
27           sel : in  STD_LOGIC_VECTOR (1 downto 0);
28           y : out  STD_LOGIC_VECTOR (3 downto 0));
29 end mux4;
30
31 architecture sequential2 of mux4 is
32 begin
33 process (x1,x2,x3,x4,sel)
34 begin
35 case sel is
36     when "00" => y<=x1;
37     when "01" => y<=x2;
38     when "10" => y<=x3;
39     when "11" => y<=x4;
40     when others => y<="XXXXX";
41 end case;
42 end process;
43 end sequential2;
```