

## Problem set 2

### 1. Write VHDL codes of the following circuits:

An 8-bit magnitude comparator using sequential as well as concurrent statements.


Don't use any kind of logical operators.

The input and output specifications are as follows:

'g' should indicate logic level "1" only when  $a > b$ , otherwise logic level "0"

'e' should indicate logic level "1" only when  $a = b$ , otherwise logic level "0"

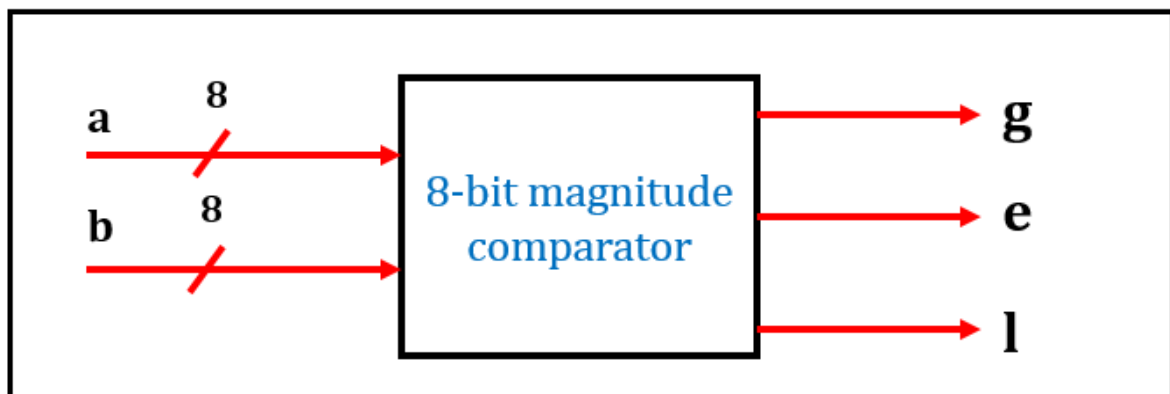'l' (Small 'L') should indicate logic level "1" only when  $a < b$ , otherwise logic level "0"



**Entity name: comparator**

**Filename should be: comparator.vhd**

2. Design a full-adder using half adders and OR gate. Use Structural modelling.