

Verilog (contd..)

Dataflow modelling

- It provides means of describing a circuit by a Boolean function rather than explicitly incorporating the gates.
- It uses different operators which act on operands to produce the desired results.
- It usually use “assign” keyword for continuous assignment. Using this assignment, a value is assigned to a net (wire).

HDL halfadder_dataflow.v - D:/codes

```
1 // Dataflow design
```

```
2
```



```
3 module halfadder_dataflow(a,b,sum,carry);
```

```
4 input a,b;
```

```
5 output sum,carry;
```

```
6 assign sum=a^b;
```

```
7 assign carry=a&b;
```

```
8 endmodule
```

```
9
```

```
module add_8bit ( input [7:0] a, b, input ci,  
                  output [7:0] s, output co );  
    assign {co, s} = a + b + ci;  
endmodule
```

(f)

2x1 MUX using DM.


```
module 2x1mux MUX-df (y, a, b, s);
```

```
output y;
```

```
input a, b, s;
```


```
assign y = (~s & a) | (s & b);
```

```
endmodule.
```

 

```
assign y = s ? b : a;
```

Problem Design a 2x4 decoder using DM.

 

E	A	B	y_3	y_2	y_1	y_0
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

$$Y_0 = E \bar{A} \bar{B}$$

$$Y_1 = E \bar{A} B$$

$$Y_2 = E A \bar{B}$$

$$Y_3 = E A B$$

module decoder_df (y, a, b, e);

output [3:0] y;

input a, b, e;

assign y[0] = (e & ~a & ~b);

assign y[1] = (e & ~a & b);

assign y[2] = (e & a & ~b);

assign y[3] = (e & a & b);

endmodule

assign y[0] = - - - ;

y[1] = - - - ;

y[2] = - - - ;

y[3] = - - - ;

②

```
module FA-def (S, cout, x, y, cin);
```

```
Output      S, cout;
```

```
input       x, y, cin;
```



```
{ assign      S = (x ^ y ^ cin);
```

```
  assign      c = ((x & y) | (y & cin) | (x & cin));
```

```
endmodule
```

→ assign {cout, S} = ~~a~~ x + y + cin.

\downarrow \downarrow
 MSB LSB

③

8-bit RCA.

```
module 8bit-RCA (input [7:0] a, b, input ci,  
                 output [7:0] s, output co);
```

```
assign {co, s} = a + b + ci;
```

endmodule. ↪ 9-bits.