

I. Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within always blocks, with subtly different behaviors.
- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
```

```
begin
```

```
x = a | b;
```

1. Evaluate $a | b$, assign result to x

```
y = a ^ b ^ c;
```

2. Evaluate $a^b c$, assign result to y

```
z = b & ~c;
```

3. Evaluate $b \& (\sim c)$, assign result to z

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
```

```
begin
```

```
x <= a | b;
```

1. Evaluate $a | b$ but defer assignment of x

```
y <= a ^ b ^ c;
```

2. Evaluate $a^b c$ but defer assignment of y

```
z <= b & ~c;
```

3. Evaluate $b \& (\sim c)$ but defer assignment of z



```
end
```

4. Assign x, y, and z with their new values

- Sometimes, as above, both produce the same result. Sometimes, not!


Why two ways of assigning values?

Conceptual need for **two kinds** of **assignment** (in `always` blocks):

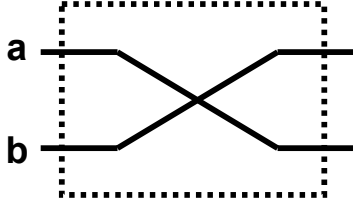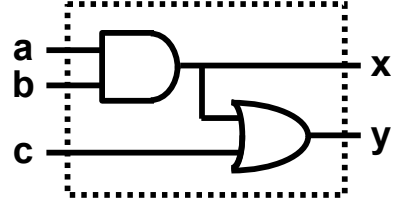		
Blocking: Evaluation and assignment are immediate	 $\begin{array}{l} a = b \\ b = a \end{array}$ 	$\begin{array}{l} x = a \ \& \ b \\ y = x \ \ c \end{array}$
Non-Blocking: Assignment is postponed until all r.h.s. evaluations are done	$\begin{array}{l} a \leq b \\ b \leq a \end{array}$	 $\begin{array}{l} x \leq a \ \& \ b \\ y \leq x \ \ c \end{array}$
When to use: (only in <code>always</code> blocks!)	Sequential Circuits	Combinational Circuits

Assignment Styles for Sequential Logic

*Flip-Flop Based
Digital Delay
Line*

 

- Will nonblocking and blocking assignments both produce the desired result?


```
module nonblocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```

Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out **simultaneously receive the old values** of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 “At each rising clock edge, $q1 = in$.
After that, $q2 = q1 = in$; After that,
 $out = q2 = q1 = in$; Finally $out = in$.”




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

Use Blocking for Combinational Logic

Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x c;	0	1	0	0	0

```
always @ (a or b or c)
begin
    x = a & b;
    y = x | c;
end
```

 

Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	

```
always @ (a or b or c)
begin
    x <= a & b;
    y <= x | c;
end
```


- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**

II. Single-clock Synchronous Circuits

We'll use Flip Flops and *Registers* – groups of FFs sharing a clock input – in a highly constrained way to build digital systems.

Single-clock Synchronous Discipline:

 
- No combinational cycles
- Single clock signal shared among all clocked devices
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!



Clocked circuit for on/off button


```
module onoff(clk,button,light) ;  
  input clk,button;  
  output light;  
  reg light;  
  always @ (posedge clk)  
  begin  
    if (button) light <= ~light;  
  end  
endmodule
```

Does this work
with a 1Mhz
CLK?

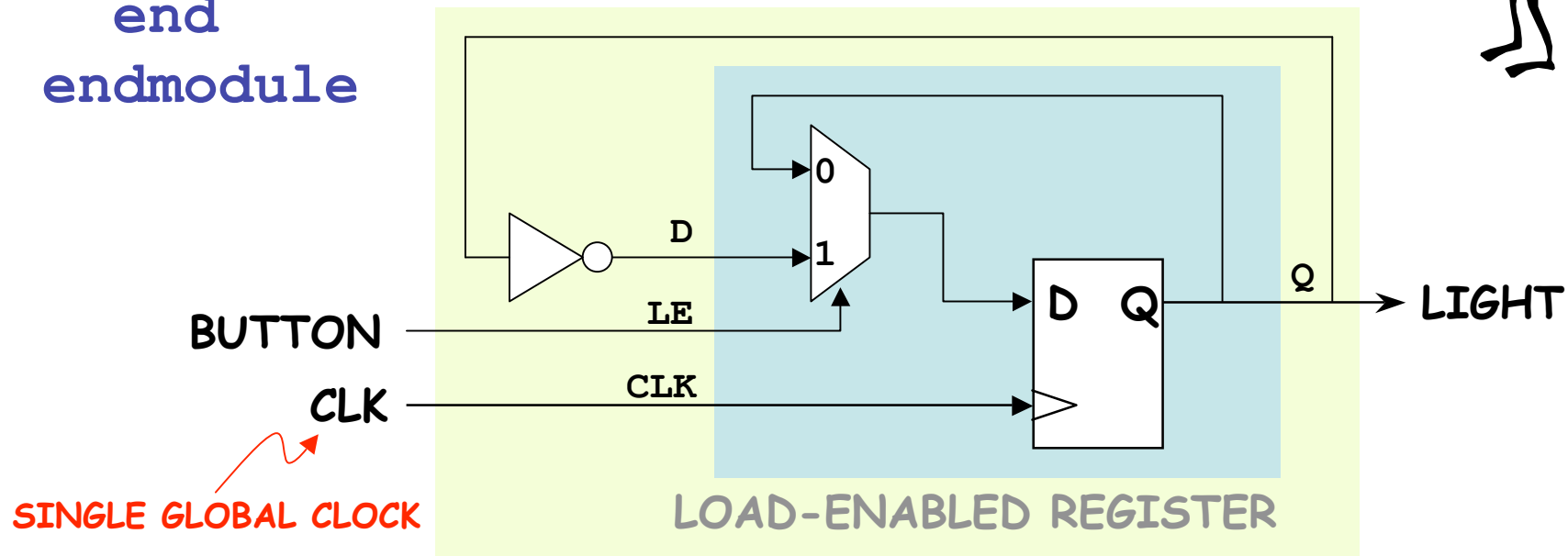


Asynchronous Inputs in Sequential Systems

What about external signals?

 

Can't guarantee setup and hold times will be met!

 When an asynchronous signal causes a setup/hold violation...





Q: Which cases are problematic?

Asynchronous Inputs in Sequential Systems

All of them can be, if more than one happens simultaneously within the same circuit.

  
*Idea: ensure that external signals directly feed **exactly one** flip-flop*



This prevents the possibility of I and II occurring in different places in the circuit, but what about metastability?

Handling Metastability

 - Preventing metastability turns out to be an impossible problem
- High gain of digital devices makes it likely that metastable conditions will resolve themselves quickly
- Solution to metastability: allow time for signals to stabilize




How many registers are necessary?

- Depends on many design parameters (clock speed, device speeds, ...)
- In 6.111, a pair of synchronization registers is sufficient


III. Finite State Machines

- Finite State Machines (FSMs) are a useful abstraction for **sequential circuits** with centralized “**states**” of operation
- At each clock edge, combinational logic computes **outputs** and **next state** as a function of **inputs** and **present state**

 


Example 1: Light Switch

- State transition diagram

 


- Logic diagram

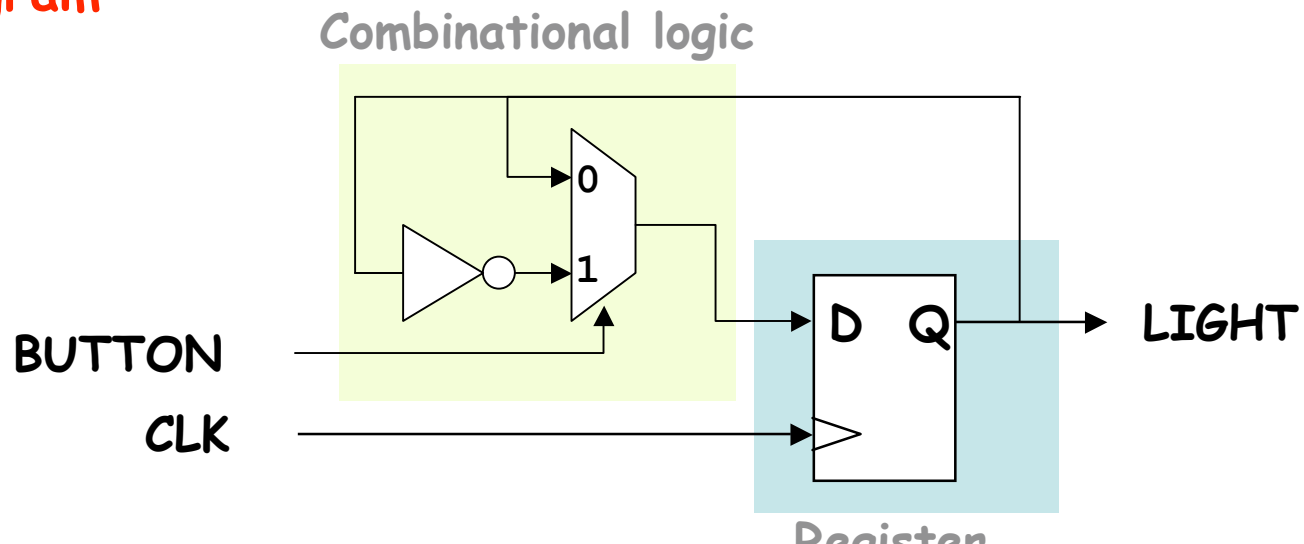

Example 2: 4-bit Counter

- Logic diagram

 


- Verilog

4-bit counter

```
module counter(clk, count);  
  input clk;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk) begin  
    count <= count+1;  
  end  
endmodule
```

Example 2: 4-bit Counter

- Logic diagram

 

- Verilog

4-bit counter with enable

```
module counter(clk,enb,count) ;
```

```
input clk,enb;
```

```
output [3:0] count;
```

```
reg [3:0] count;
```

```
always @ (posedge clk) begin
```

```
count <= enb ? count+1 : count;
```

```
end
```

```
endmodule
```


Could I use the following instead?

```
if (enb) count <= count+1;
```



Example 2: 4-bit Counter

- Logic diagram

 

- Verilog

4-bit counter with enable and synchronous clear

```
module counter(clk,enb,clr,count) ;
```

```
    input  clk,enb,clr;
```

```
    output [3:0] count;
```

```
    reg [3:0] count;
```

```
    always @ (posedge clk) begin
```

```
        count <= clr ? 4'b0 : (enb ? count+1 : count);
```

```
    end
```

```
endmodule
```


*Isn't this a lot like
Exercise 1 in Lab 2?*




Two Types of FSMs

Moore and Mealy FSMs : different output generation

- Moore FSM:

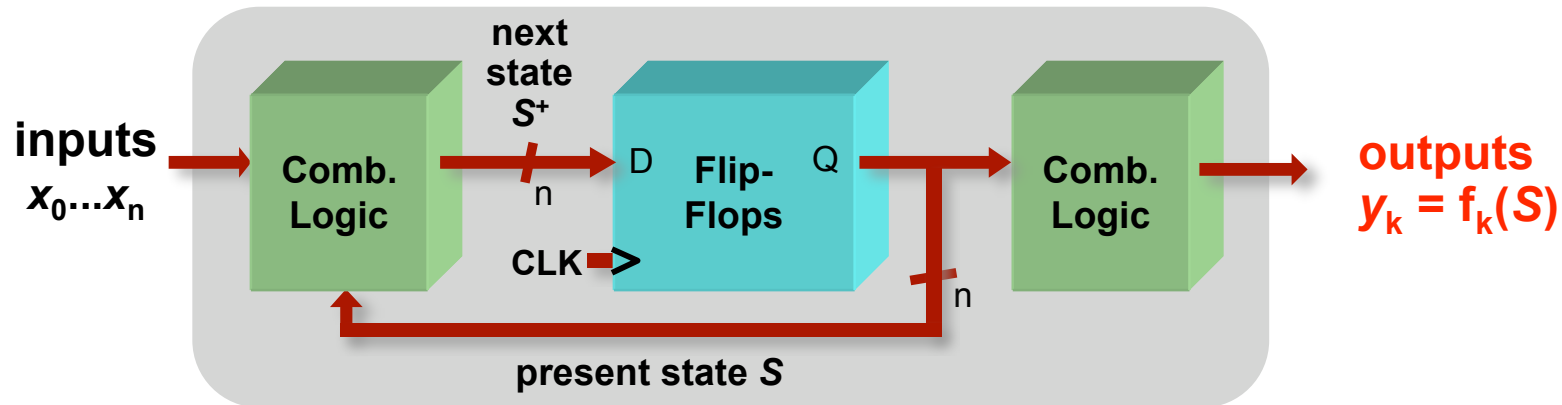


- Mealy FSM:

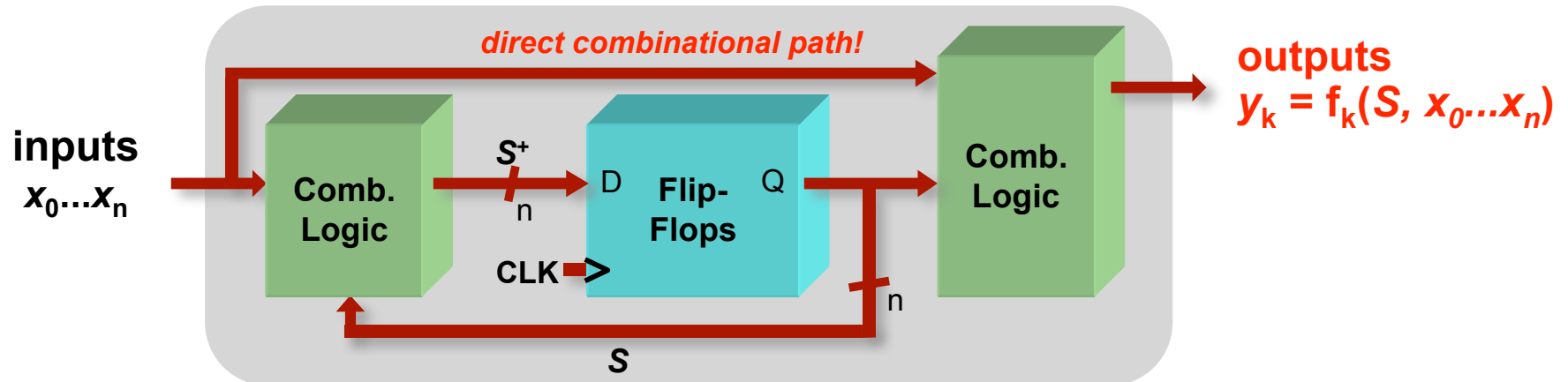


Design Example: Level-to-Pulse

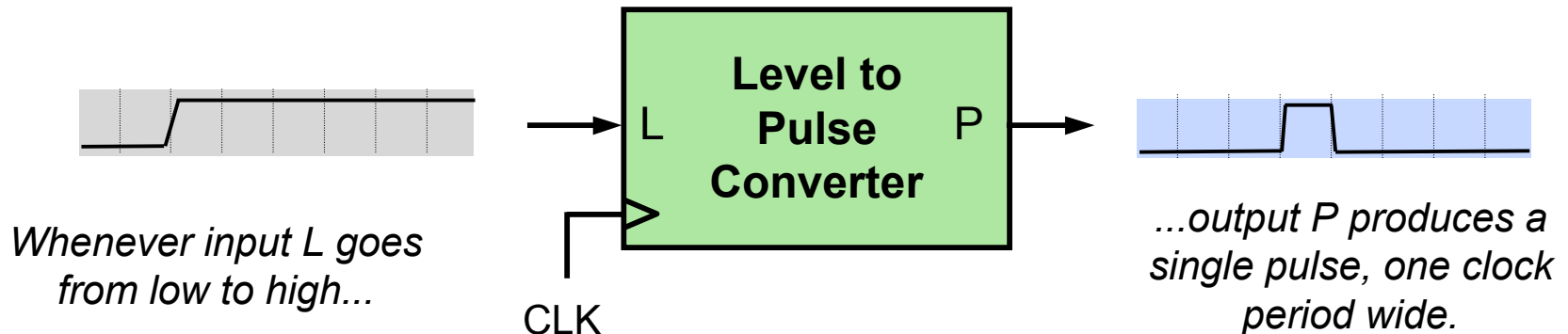- A **level-to-pulse converter** produces a single-cycle pulse each time its input goes high.
- It's a synchronous rising-edge detector.
- Sample uses:
 - Buttons and switches pressed by humans for arbitrary periods of time
 - Single-cycle enable signals for counters




Step 1: State Transition Diagram

- Block diagram of desired system:

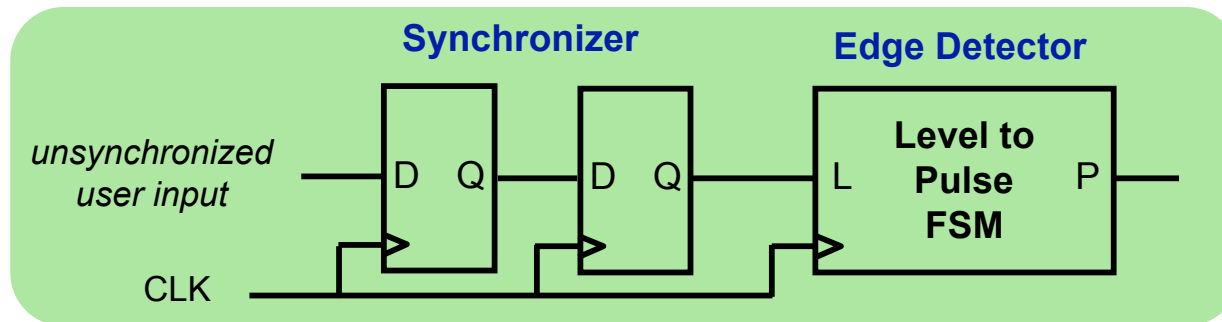


 - State transition diagram** is a useful FSM representation and design aid:




Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

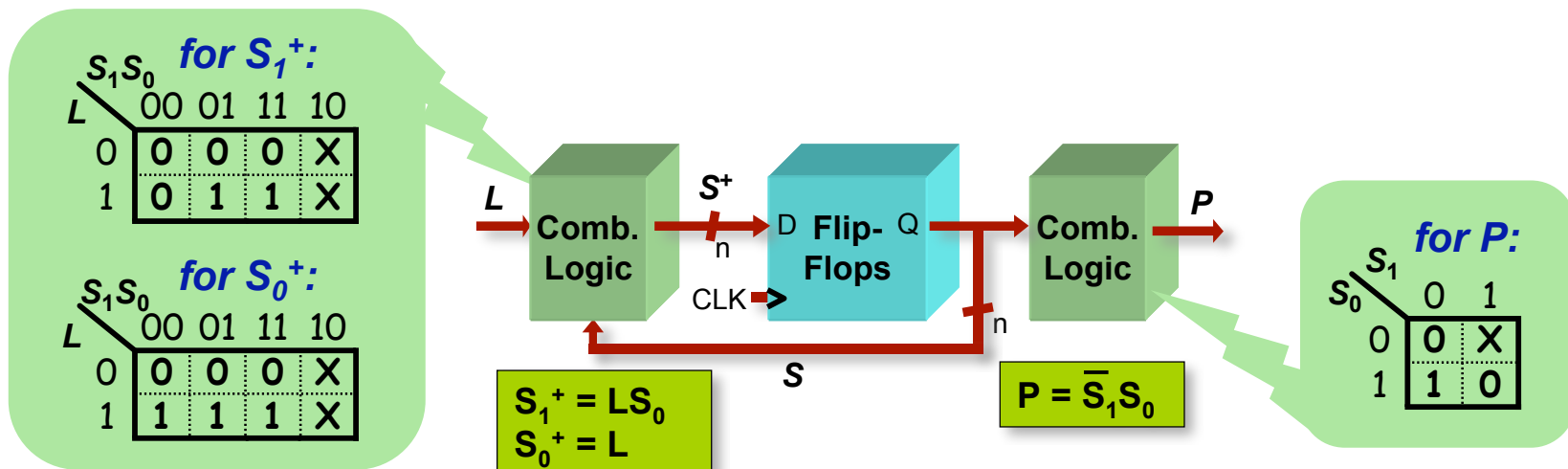
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

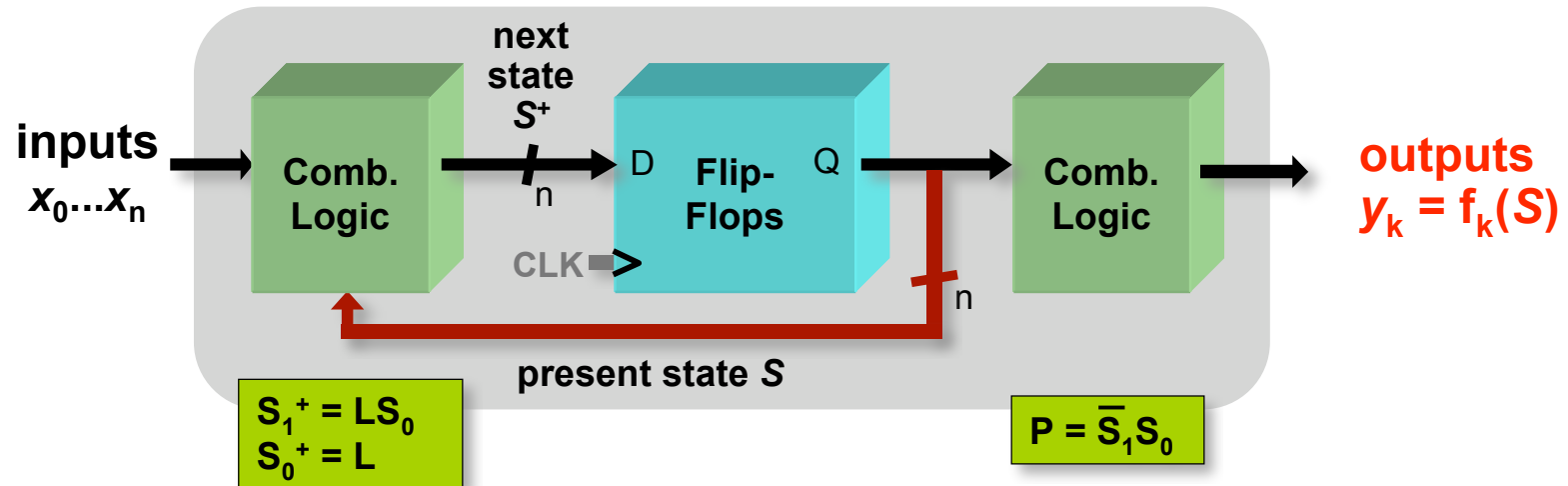

 
Moore FSM circuit implementation of level-to-pulse converter:




Design of a Mealy Level-to-Pulse

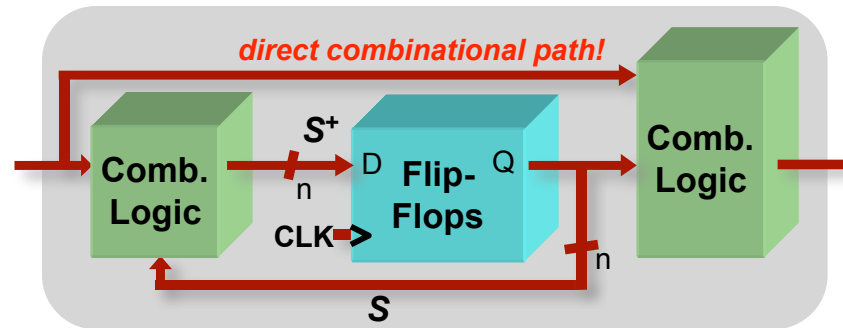

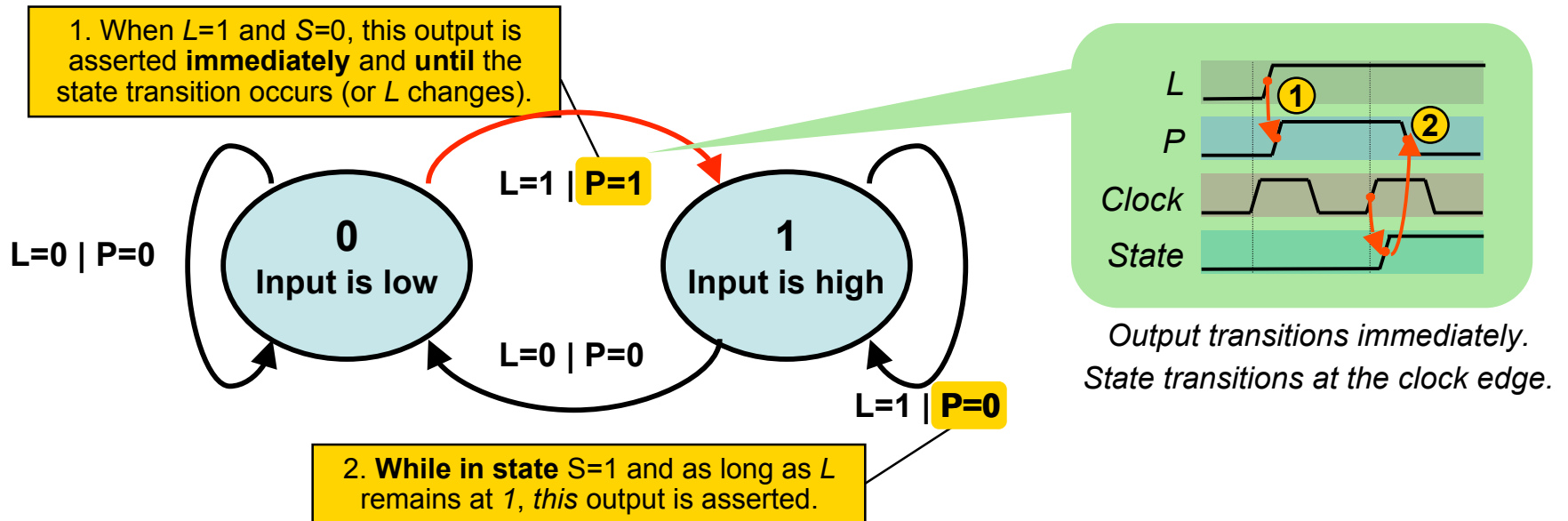- Since outputs are determined by state *and* inputs, Mealy FSMs may need fewer states than Moore FSM implementations




Mealy Level-to-Pulse Converter

 

Pres. State	In	Next State	Out
S	L	S^+	P
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	0

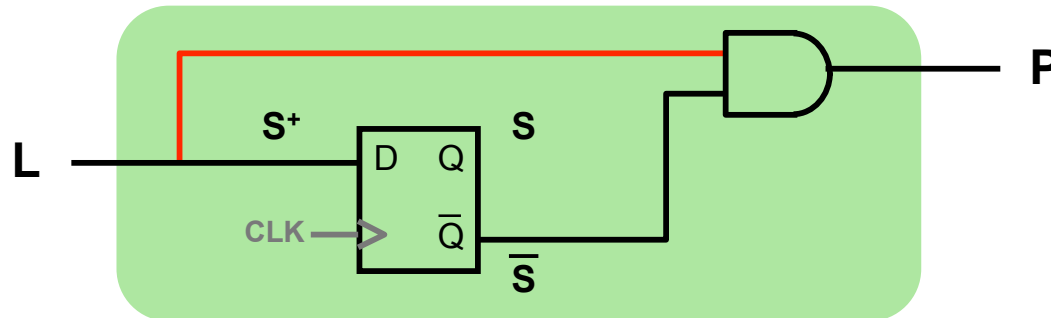Mealy FSM circuit implementation of level-to-pulse converter:




- FSM's state simply remembers the previous value of L
- Circuit benefits from the Mealy FSM's implicit single-cycle assertion of outputs during state transitions


Moore/Mealy Trade-Offs

- How are they different?
 - Moore: **outputs** = $f(\text{state})$ only
 - Mealy **outputs** = $f(\text{state} \text{ and } \text{input})$
 - Mealy outputs generally occur one cycle earlier than a Moore:

Moore: delayed assertion of P

 

Mealy: immediate assertion of P

 

- Compared to a Moore FSM, a Mealy FSM might...
 - Be more difficult to conceptualize and design
 - Have fewer states

Light Switch Revisited

