

# State Machine

- It is a **concept** which can be employed to design any digital system in a **generalized way**.
- State machine is a system or circuit which has several states in which it can exist and **it may have clearly defined a set of inputs** which will steer the system from one state to another state and **each state also may produce an output**.

# Characteristics of state machine:


- The next state of state machine always depends on previous state.
- There may be or may not be external inputs
- There will be definitely output. However, the state itself may be the output.
- In general, the behavior of the circuit depends on the present state and external inputs (optional).

# Synchronous state machine

- Transition triggered by CLK
- Transition is determined by present state and may be also by external inputs.
- State transition is not necessary in each clock period.
- Output will be determined by the present state and external inputs.

Next\_state = func(present\_state, ext. inputs)  
Output = func(present\_state, ext. inputs)


# State diagram:

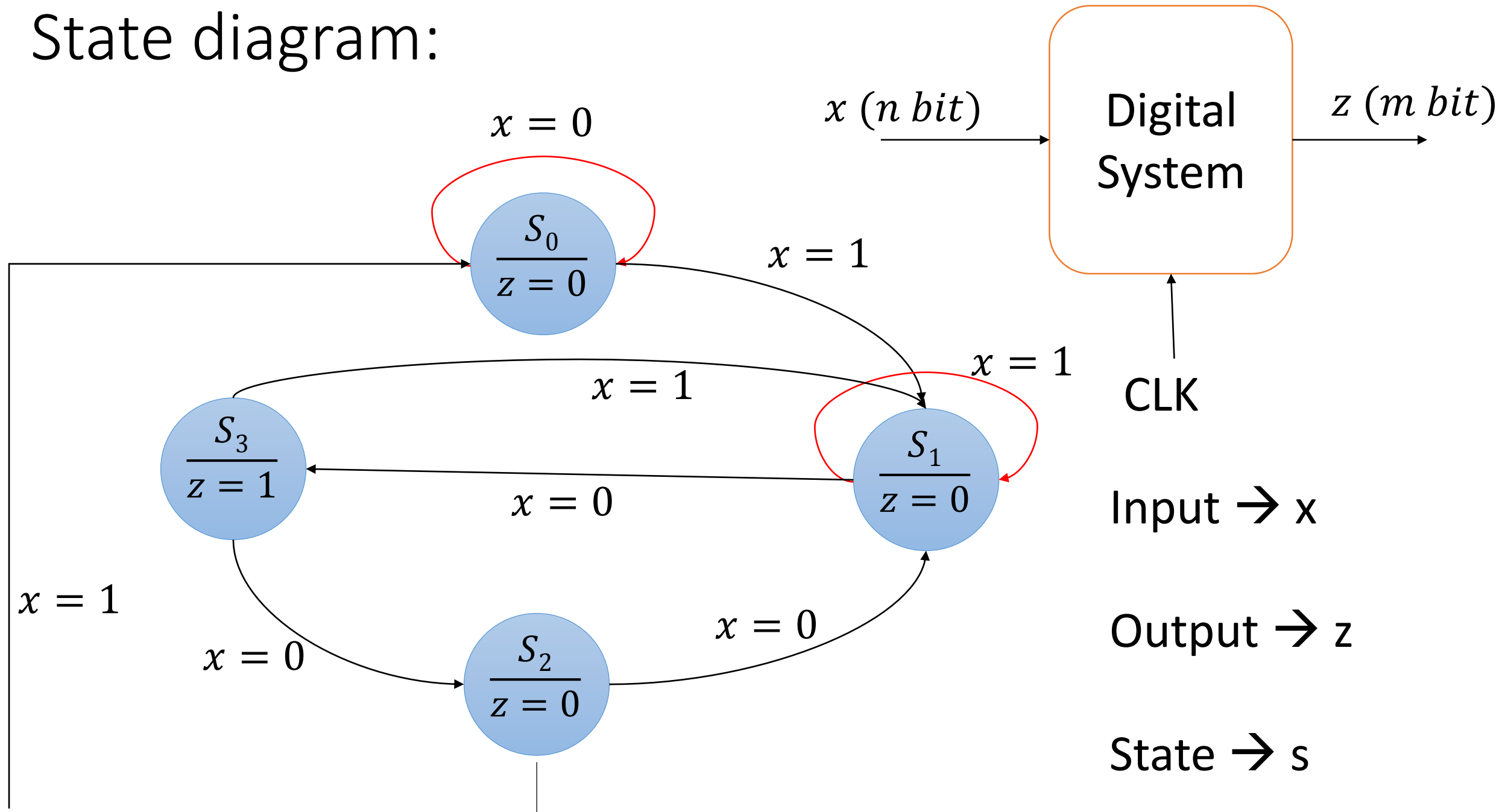

# Generalized model of state machine

4 states

2 state variables  $\rightarrow A B$

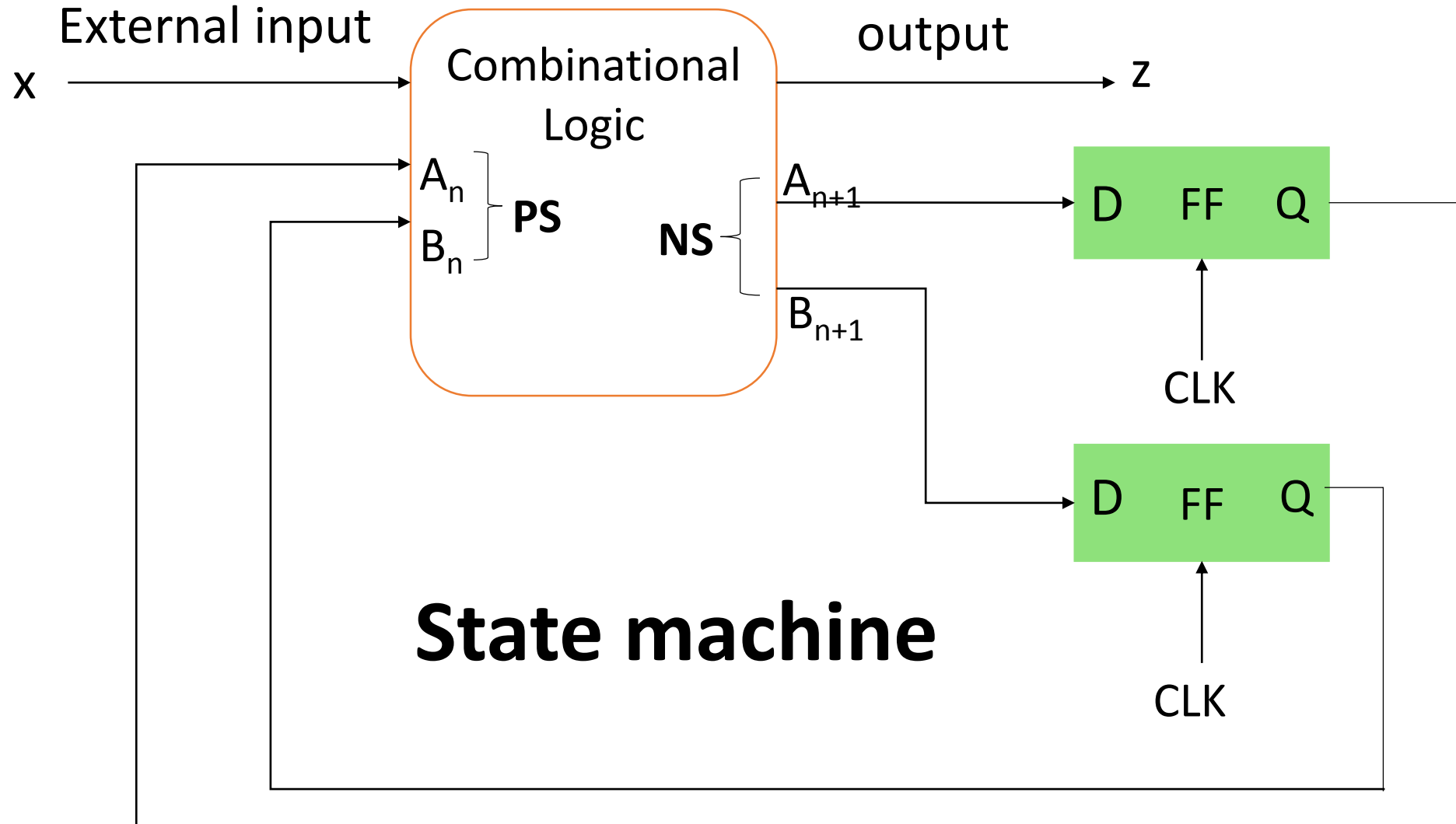

# Takeaway Points:

Any digital system can be modelled as a state machine


1. Combinational circuit (with one state)
2. Flip-flop (Two states)
3. Counter




**State machine**

# Special scenario: Counter $\rightarrow$ State machine

- Lets consider a 3 bit (mod-6 counter)

 


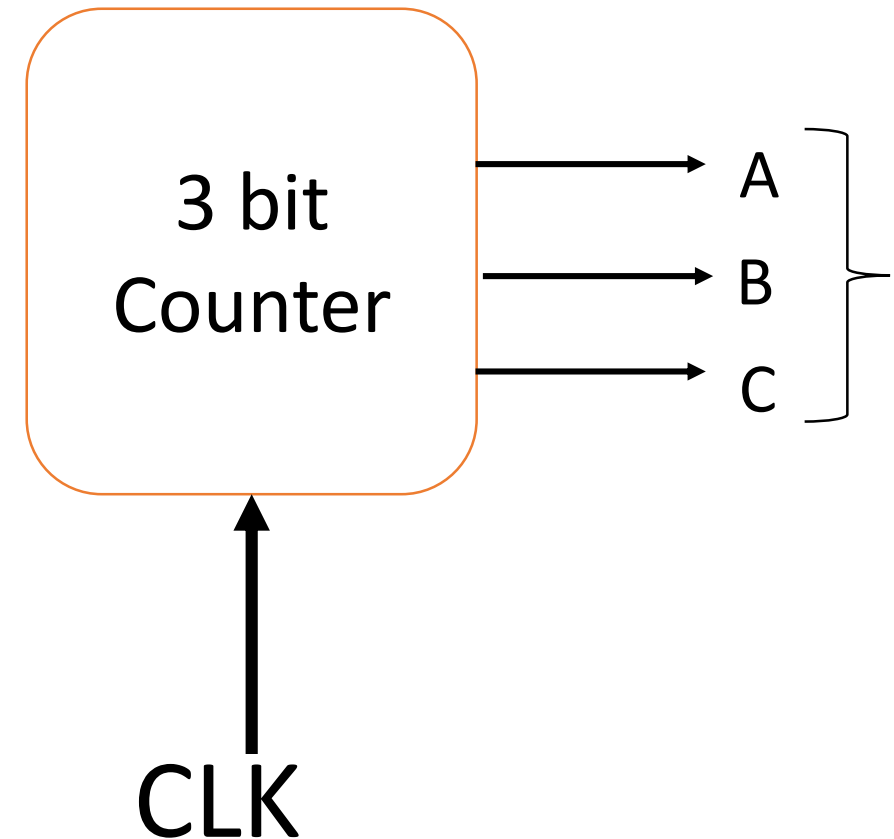No external inputs  
State variables  $\rightarrow$  output


 
# Design strategy: State machine

- **Step 1:** System/circuit behavior will be given to you as a specification.
- **Step 2:** Represent the given model specification using a state diagram (graph).
- **Step 3:** Implement the state graph using hardware.






# Summary

- State machine: **A design methodology**
- **Synchronous state machine** → triggered by clock. However, circuit may stay at the same state for many clock cycle.
- A state machine may not have external input and output. Eg. Counter
- Asynchronous state machine → **triggered by event**. A little more difficult to analyze.
- Next we will look at how the given state graph can be translated into a hardware model.

# State diagram: Moore Machine

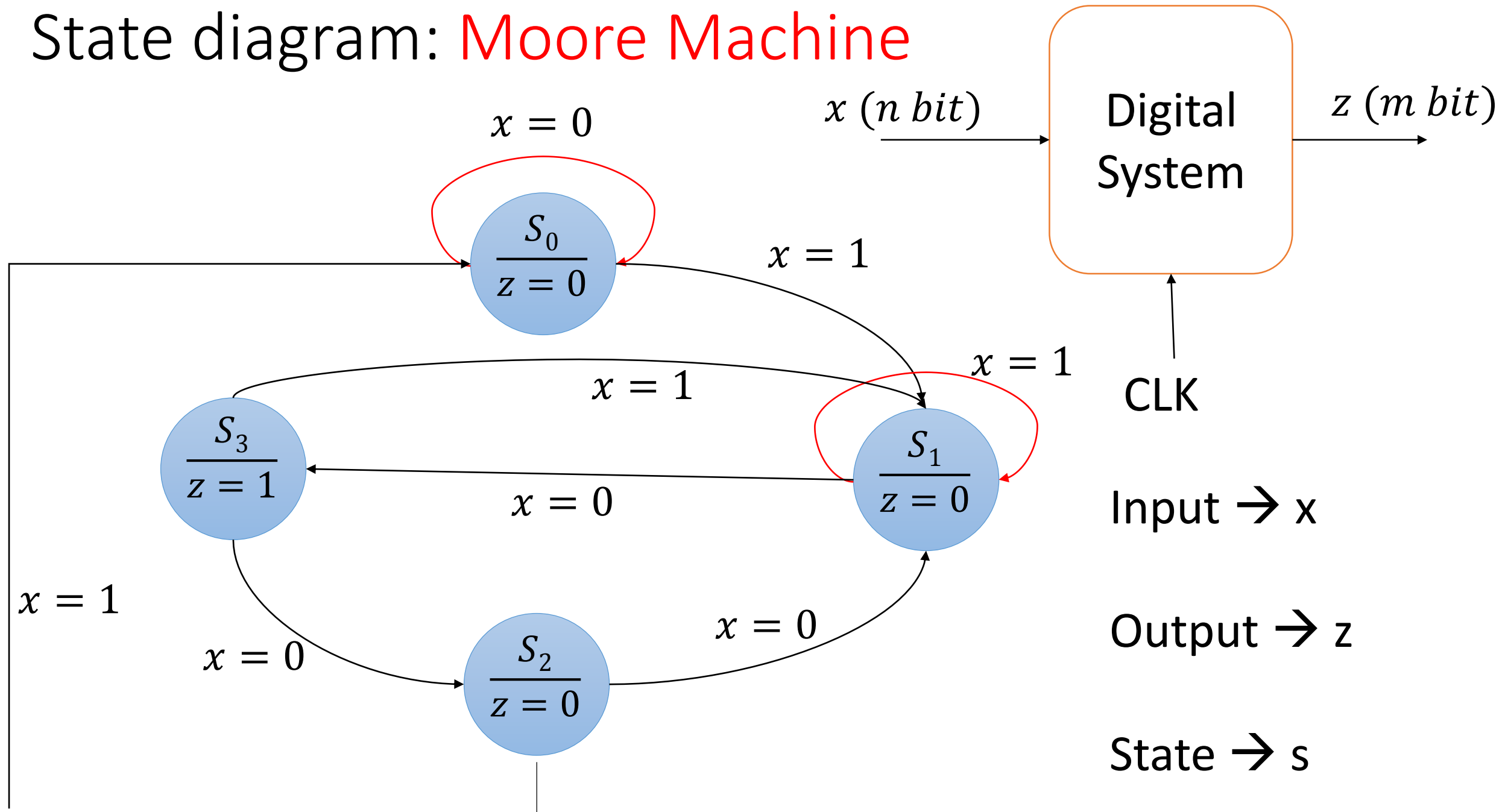

State table of the state-diagram shown in last slide

State variables AB

$S_0 \rightarrow 00$


$S_1 \rightarrow 01$

$S_2 \rightarrow 10$

$S_3 \rightarrow 11$

Present state (AB)	Input (X)	Next state (A'B')	Output (Z)
00	0	00	0
00	1	01	0
01	0	11	0
01	1	01	0
10	0	01	0
10	1	00	0
11	0	10	1
11	1	01	1

# State diagram: Mealy Machine

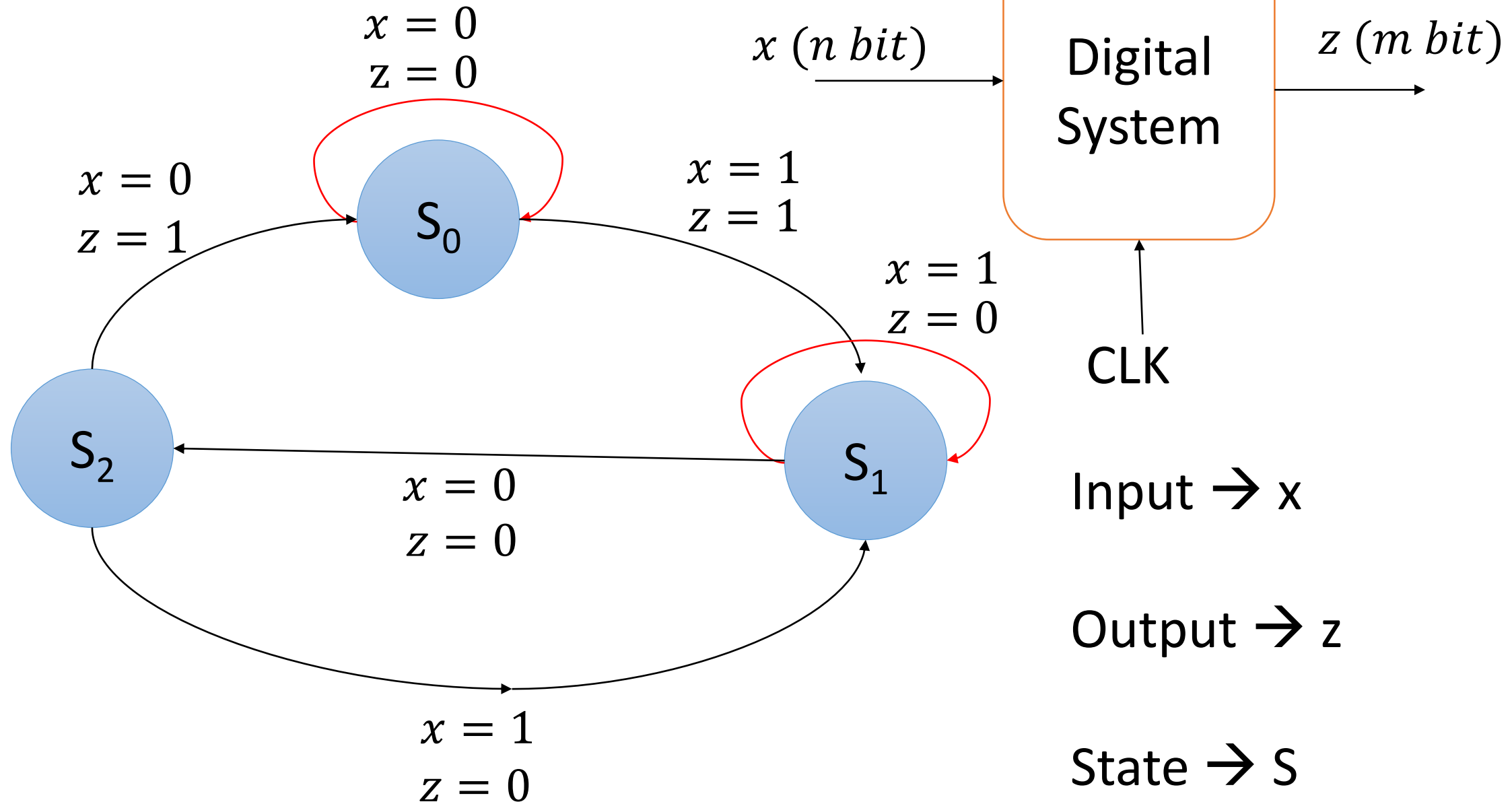

State table of the state-diagram shown in last slide

State variables AB

$S_0 \rightarrow 00$

$S_1 \rightarrow 01$

$S_2 \rightarrow 10$

Present state (AB)	Input (X)	Next state (A'B')	Output (Z)
00	0	00	0
00	1	01	1
01	0	10	0
01	1	01	0
10	0	00	1
10	1	01	0
11	X	XX	0
11	X	XX	0

# Summary

- State machine can be classified into two sub-classes based on the output.
- Steering combinational logic for computing the output will be determined as:

Output = func(present\_state, ext. inputs)

➡ Mealy machine

Output = func(present\_state)

➡ Moore machine