

# Digital filter

Delay modelling

## Problem: 4-Point Moving Average (MA4) Filter in RTL

### Goal:

Design and verify a synchronous RTL module that smooths a discrete-time input sequence  $x[n]$  by replacing each sample with the average of itself and the previous three samples:


$$y[n] = \frac{x[n] + x[n - 1] + x[n - 2] + x[n - 3]}{4}.$$

Clock	x_in	x1	x2	x3	y_out = (x_in+x1+x2+x3)/4
1	10	0	0	0	2
2	20	10	0	0	7
3	15	20	10	0	11
4	25	15	20	10	17
5	20	25	15	20	20
6	10	20	25	15	17

## ✓ Interpretation

- During the **first (N-1) = 3 clock cycles**, the filter **has not yet “filled”** its memory window.
- From the **4th clock onward**, it produces **true averages** over 3 valid samples.

Clock	x_in	x1	x2	x3	y_out = (x_in+x1+x2+x3)/4
1	10	0	0	0	2
2	20	10	0	0	7
3	15	20	10	0	11
4	25	15	20	10	17
5	20	25	15	20	20
6	10	20	25	15	17

 

```
module moving_avg_4_filter (  
    input  wire      clk,  
    input  wire      rst,  
    input  wire [7:0] x_in,  
    output reg  [7:0] y_out  
);  
    // Shift registers for previous samples  
    reg [7:0] x1, x2, x3;  
  
    wire [9:0] sum;  
  
    wire [7:0] avg;  
    .....
```

*// Intermediate sum (max  $4*255=1020$  -> needs 10 bits)*

**assign** sum = x\_in + x1 + x2 + x3;

*// Average (integer division by 4 using right shift)*

**assign** avg = sum >>2;

```
// Intermediate sum (max 4*255=1020 -> needs 10 bits)  
assign sum = x_in + x1 + x2 + x3;  
  
// Average (integer division by 4 using right shift)  
assign avg = sum[9:2];
```



```
// Sequential logic: update registers and output  
always @(posedge clk) begin  
    if (rst) begin  
        x1 <= 0;  
        x2 <= 0;  
        x3 <= 0;  
        y_out <= 0;  
    end else begin  
        x3 <= x2;  
        x2 <= x1;  
        x1 <= x_in;  
        y_out <= avg;  
    end  
end  
endmodule
```

**Write the code for Parameterized 4-Point Moving Average Filter**  
**Unsigned N-bit input, output each clock**

## **\*\*Concatenation Operator { , }**

verilog

{A, B, C, ...}

Concatenation means joining signals or constants end-to-end (bitwise).

### ◆ Example 1 – Join two 4-bit values

verilog

```
wire [3:0] upper = 4'b1010;  
wire [3:0] lower = 4'b1100;  
  
wire [7:0] combined = {upper, lower};
```

**Result:**

ini

```
combined = 8'b10101100
```

It literally **glues** the bits of `upper` and `lower` together.

## ◆ Example 2 – Combine different sizes

verilog

```
wire [1:0] a = 2'b11;  
wire [2:0] b = 3'b010;  
wire [4:0] c = {a, b}; // total 5 bits
```

**Result:**

ini

```
c = 5'b11010
```

So {a,b} → first bits of a, then bits of b.

## **\*\*Replication Operator** {N{expression}}

```
verilog
```

```
{N{expression}}
```

Replication means **repeat** an expression N times and **concatenate** the results.

---

### ◆ **Example 1 – Make all zeros or ones**

```
verilog
```

```
wire [7:0] all_zero = {8{1'b0}};    // 8 zeros: 00000000  
wire [7:0] all_ones = {8{1'b1}};    // 8 ones : 11111111
```

## ◆ Example 2 – Repeat a 2-bit pattern

verilog

```
wire [7:0] pattern = {4{2'b10}};
```

**Result:**

ini

```
pattern = 8'b10101010
```

So `{4{2'b10}}` → `2'b10` repeated 4 times.

### ◆ Example 3 – Combine replication and concatenation

verilog

```
wire [11:0] mix = {{3{2'b01}}}, 2'b11};
```



### ◆ Example 3 – Combine replication and concatenation

verilog

```
wire [11:0] mix = {{3{2'b01}}}, 2'b11};
```

#### Steps:

- $\{3\{2'b01\}\} \rightarrow 2'b01 \ 2'b01 \ 2'b01 = 6'b010101$
- Then add  $2'b11$
- Final result:  $8'b01010111$

Operator	Syntax	Purpose	Example	Result
Concatenation	{a, b, c}	Joins signals end-to-end	{4'b1100, 4'b0011}	8'b11000011
Replication	{N{expr}}	Repeats an expression N times	{4{2'b10}}	8'b10101010

Method	Syntax Example
Decimal zero	<code>a = 8'd0;</code>
Binary	<code>a = 8'b00000000;</code>
Hex	<code>a = 8'h00;</code>
Replication	<code>a = {8{1'b0}};</code>
Concatenation	<code>a = {1'b0,1'b0,...};</code>

```

module moving_avg_4_param #(
    parameter integer WIDTH = 8    // input/output width
) (
    input  wire          clk,
    input  wire          rst,      // synchronous active-high reset
    input  wire [WIDTH-1:0] x_in,  // current input
    output reg [WIDTH-1:0] y_out   // averaged output
);

    // Delay elements
    reg [WIDTH-1:0] x1, x2, x3;

    // Sum width = WIDTH + log2(4) = WIDTH + 2
    wire [WIDTH+1:0] sum = x_in + x1 + x2 + x3;

    // Divide by 4 → right-shift by 2 bits (hardware-efficient) |
    wire [WIDTH-1:0] avg = sum>>2;

    // Sequential update
    always @(posedge clk) begin
        if (rst) begin
            x1    <= {WIDTH{1'b0}};
            x2    <= {WIDTH{1'b0}};
            x3    <= {WIDTH{1'b0}};
            y_out <= {WIDTH{1'b0}};
        end else begin
            x3    <= x2;
            x2    <= x1;
            x1    <= x_in;
            y_out <= avg;
        end
    end
end
endmodule

```

## Problem Statement:

You are required to design a **4-stage shift register** in Verilog.

The circuit should accept an **8-bit parallel input** `data_in` and output the data after it passes through **four flip-flops connected in series**.

At every positive clock edge:

- The first register should capture the current input ( `data_in` ).
- Each subsequent register should capture the value of the previous register from the **previous clock cycle**.

The reset should be **synchronous** and active-high.

When reset is active, all registers must be cleared to 0.

## Behavioral Description:

- Use four internal 8-bit registers `r0`, `r1`, `r2`, `r3`.
- Use **non-blocking assignments** (`<=`) for sequential updates.
- The output `data_out` should be connected to the output of the last register (`r3`).

## Hint:

Each register represents one clock-cycle delay, so:

$$\text{data\_out}(n) = \text{data\_in}(n - 3)$$

Clock:	↑	↑	↑	↑	↑	↑	↑
Input x:	x0	x1	x2	x3	x4	x5	x6
Output y:	--	--	--	x0	x1	x2	x3
				<--- 3-clock delay --->			

Clock Cycle (n)	Input data_in = x(n)	r0	r1	r2	r3	data_out (= r3)
0 (Reset)	—	0	0	0	0	0
1	x(0)	x(0)	0	0	0	0
2	x(1)	x(1)	x(0)	0	0	0
3	x(2)	x(2)	x(1)	x(0)	0	0
4	x(3)	x(3)	x(2)	x(1)	x(0)	x(0)
5	x(4)	x(4)	x(3)	x(2)	x(1)	x(1)
6	x(5)	x(5)	x(4)	x(3)	x(2)	x(2)
7	x(6)	x(6)	x(5)	x(4)	x(3)	x(3)
8	x(7)	x(7)	x(6)	x(5)	x(4)	x(4)

Now replace all non-blocking assignments ( `<=` ) with blocking assignments ( `=` ) inside the `always` block and simulate again.

verilog

 Copy code

```
r0 = data_in;  
r1 = r0;  
r2 = r1;  
r3 = r2;
```



Assignment Type	Behavior	Output Relation
Non-blocking ( <code>&lt;=</code> )	Sequential delay pipeline	<code>data_out = x(n-3)</code>
Blocking ( <code>=</code> )	Cascaded combinational update	<code>data_out = x(n)</code>

- $x[n]$  = value of `data_in` at clock cycle  $n$ ,  
then:

Register	Contents after clock $n$	Expression
<code>r0[n]</code>	current input	<code>x[n]</code>
<code>r1[n]</code>	previous input	<code>x[n-1]</code>
<code>r2[n]</code>	input two cycles ago	<code>x[n-2]</code>
<code>r3[n]</code>	input three cycles ago	<code>x[n-3]</code>
<code>data_out[n]</code>	—	<code>x[n-3]</code>

## Problem Statement

Design a **sequential circuit** in Verilog to generate the **Fibonacci number sequence**.


The Fibonacci sequence is defined as:

$$F_0 = 0, \quad F_1 = 1, \quad F_n = F_{n-1} + F_{n-2} \text{ for } n \geq 2$$

Your Verilog module should use **two registers** to store the previous two numbers and compute the next Fibonacci number at **each positive clock edge**.

Clock	a	b	fib_out (next = a + b)
Reset	0	1	0
1	0	1	1
2	1	1	2
3	1	2	3
4	2	3	5
5	3	5	8
6	5	8	13

# FIR Direct Form

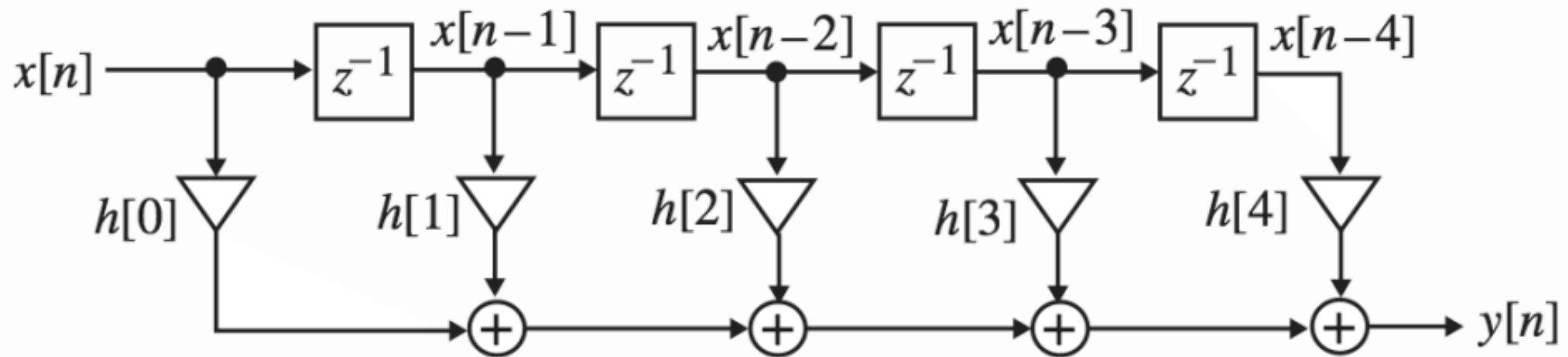

# FIR Direct Form Transposed

